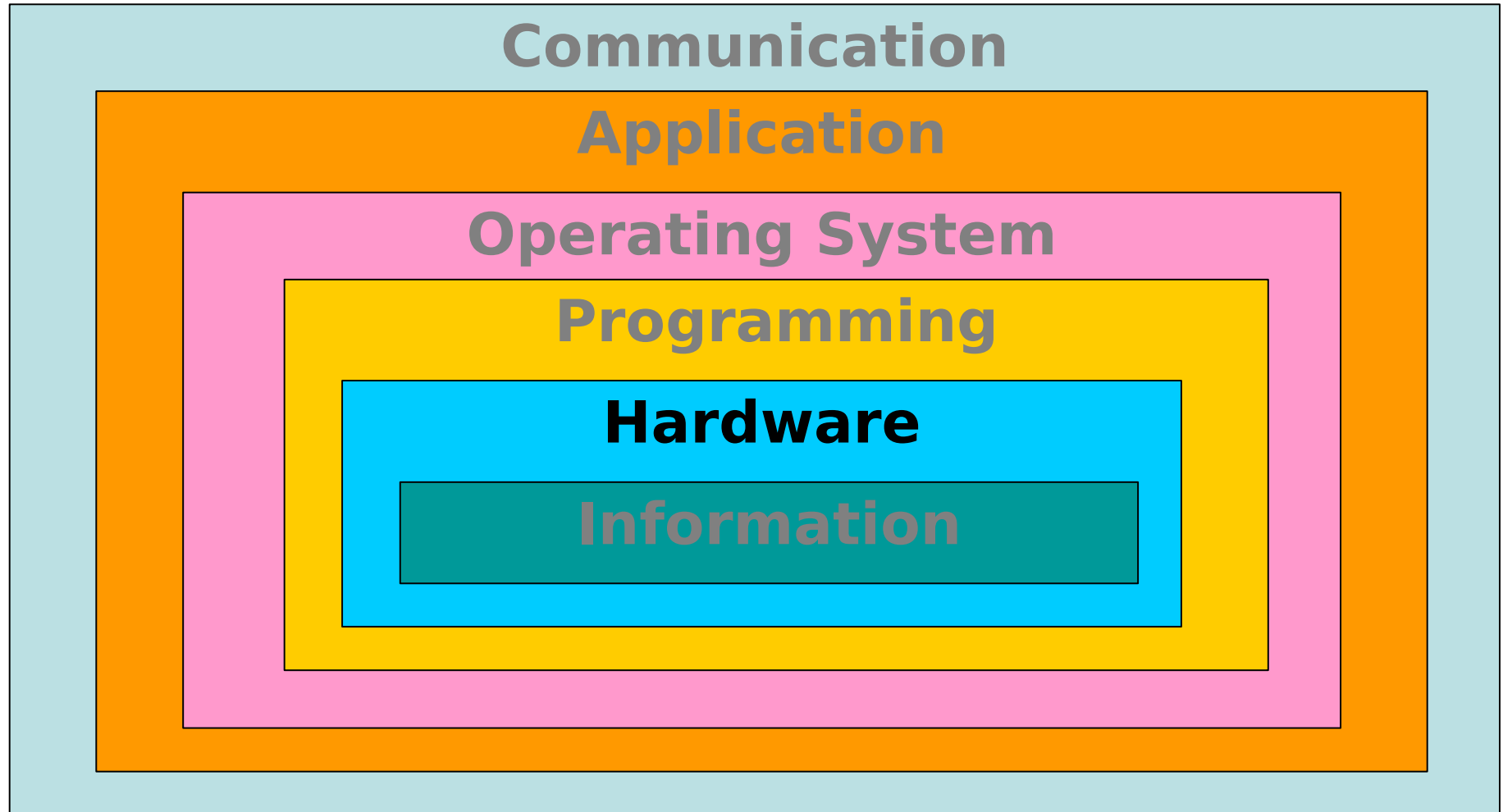


# Chapter 4

## Gates and Circuits



# Layers of a Computing System



# Chapter Goals

- Identify the basic **gates** and describe the behavior of each
- Describe how gates are **implemented** using transistors
- Combine basic **gates into circuits**
- Describe the **behavior** of a gate or circuit using **Boolean expressions, truth tables, and logic diagrams**

# Computers and Electricity

- **Gate** - A device that performs a basic operation on electrical signals
- **Circuits** - Gates combined to perform more complicated tasks

# Computers and Electricity

- There are **three** different, but equally powerful, notational methods for describing the behavior of gates and circuits
  - **Boolean expressions**
  - **logic diagrams**
  - **truth tables**

# Computers and Electricity

- **Boolean expressions** Expressions in **Boolean algebra**, a mathematical notation for expressing two-valued logic

This algebraic notation is an elegant and powerful way to **demonstrate the activity** of electrical circuits

# Computers and Electricity

- **Logic diagram** A graphical representation of a circuit
  - Each type of gate is represented by a specific **graphical symbol**
- **Truth table** A table showing **all possible input value** and the associated **output values**

# Gates

- Let's examine the processing of the following **six types** of gates
  - **NOT**
  - **AND**
  - **OR**
  - **XOR**
  - **NAND**
  - **NOR**
- Typically, logic **diagrams** are black and white, and the gates are **distinguished** only by their **shape**



# NOT Gate

- A **NOT** gate accepts **one input** value and produces **one output** value

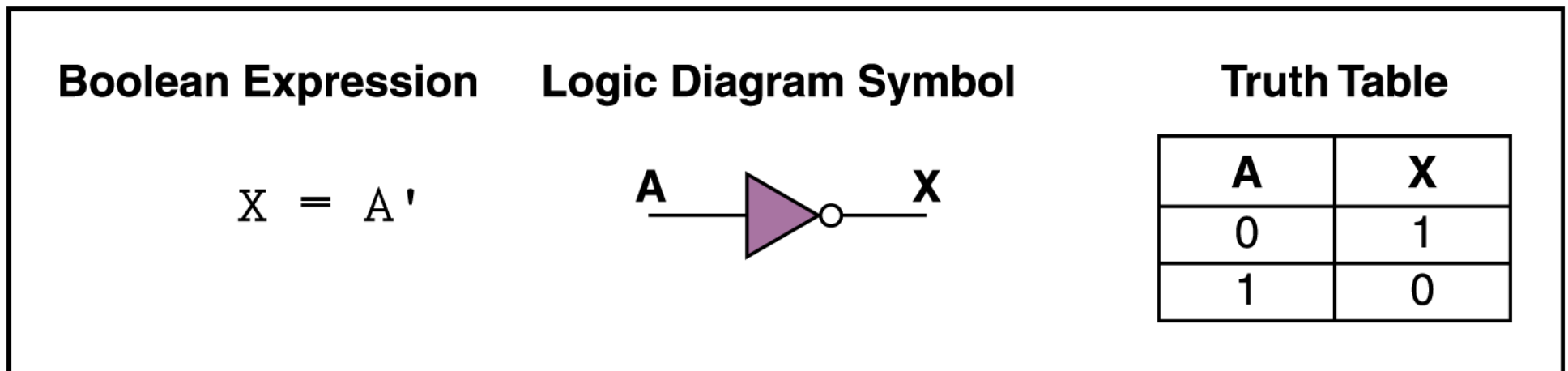


Figure 4.1 Various representations of a NOT gate

# NOT Gate

- By definition, if the input value for a NOT gate is 0, the output value is 1, and if the input value is 1, the output is 0
- A NOT gate is sometimes referred to as an *inverter* because it inverts the input value

# AND Gate

- An **AND** gate accepts two input signals
- If the **two input values** for an AND gate are **both 1**, the **output is 1**; **otherwise**, the output is **0**

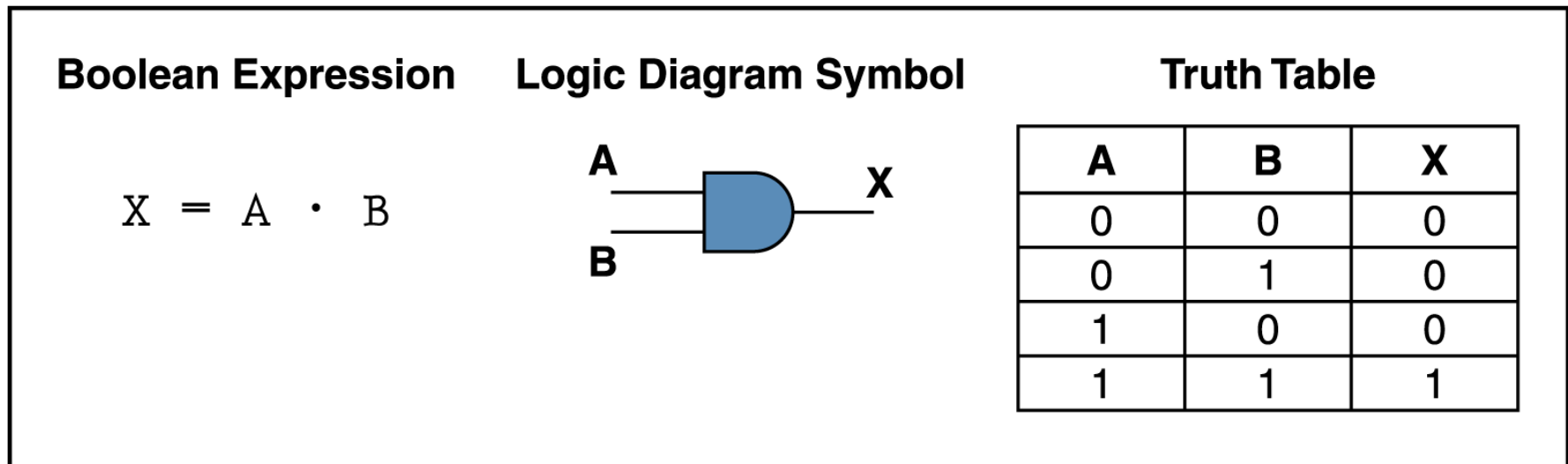


Figure 4.2 Various representations of an AND gate

# OR Gate

- If the **two input values** are **both 0**, the **output value is 0**; otherwise, the **output is 1**

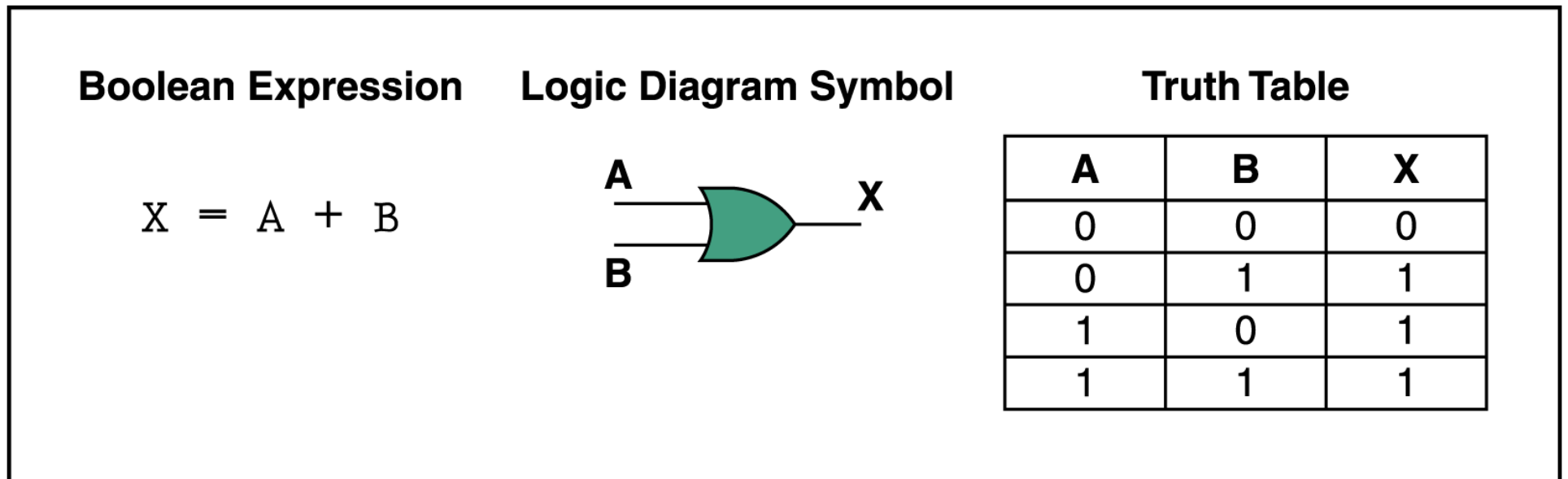


Figure 4.3 Various representations of a OR gate

# XOR Gate

- **XOR**, or *exclusive* OR, gate
  - An XOR gate produces 0 if its two inputs are the same, and a 1 otherwise
  - Note the difference between the XOR gate and the OR gate; they differ only in one input situation
  - When both input signals are 1, the OR gate produces a 1 and the XOR produces a 0

# XOR Gate

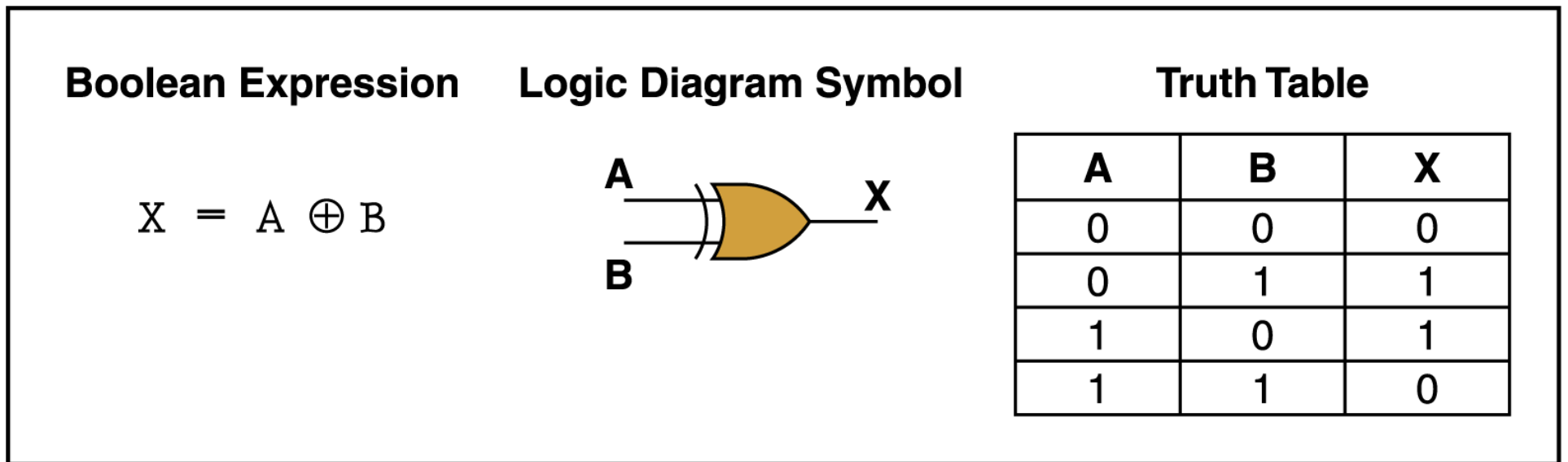


Figure 4.4 Various representations of an XOR gate

# NAND and NOR Gates

- The **NAND** and **NOR** gates are essentially the opposite of the AND and OR gates, respectively

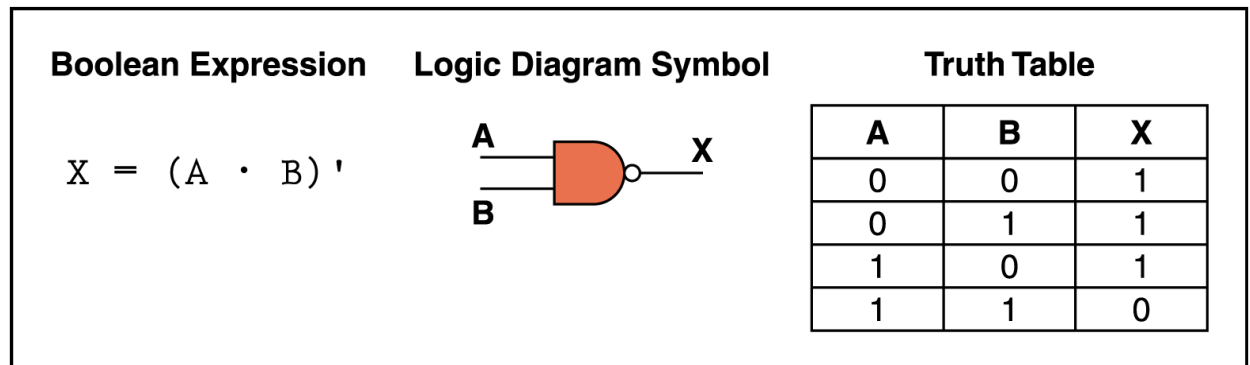


Figure 4.5 Various representations of a NAND gate

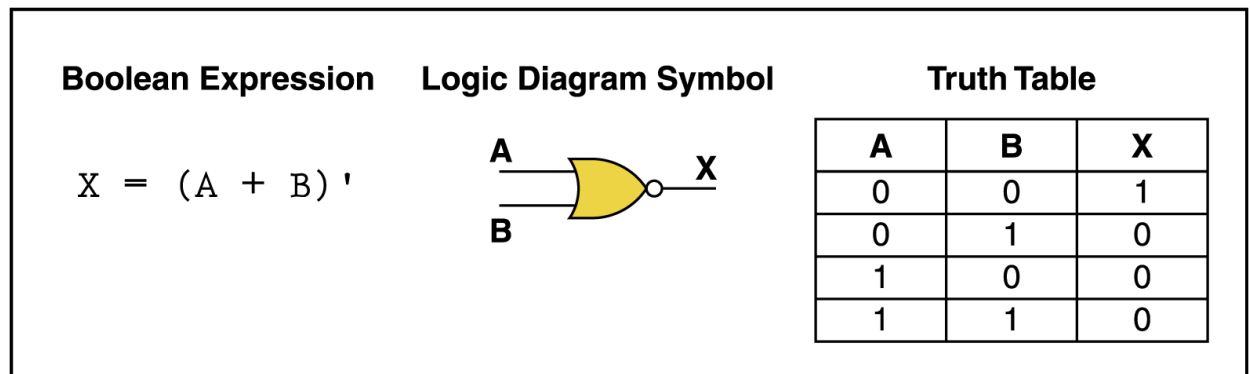


Figure 4.6 Various representations of a NOR gate

# Review of Gate Processing

- A **NOT** gate *inverts* its *single input* value
- An **AND** gate produces **1** if *both input values* are **1**
- An **OR** gate produces **1** if *one or the other or both* input values are **1**




# Review of Gate Processing

- An **XOR** gate produces **1** if **one or the other** (but not both) **input** values are **1**
- A **NAND** gate produces the **opposite** results of an **AND** gate
- A **NOR** gate produces the **opposite** results of an **OR** gate

# Gates with More Inputs

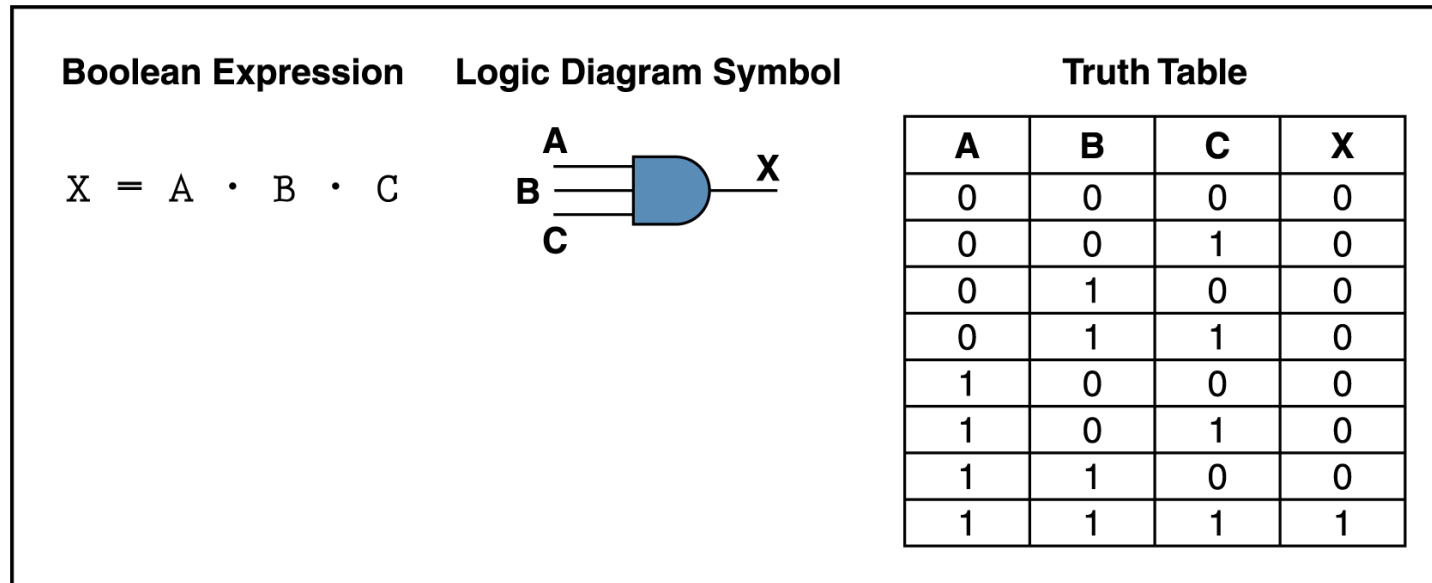- Gates can be designed to accept **three or more input** values
- A three-input AND gate, for example, produces an output of 1 only if all input values are 1


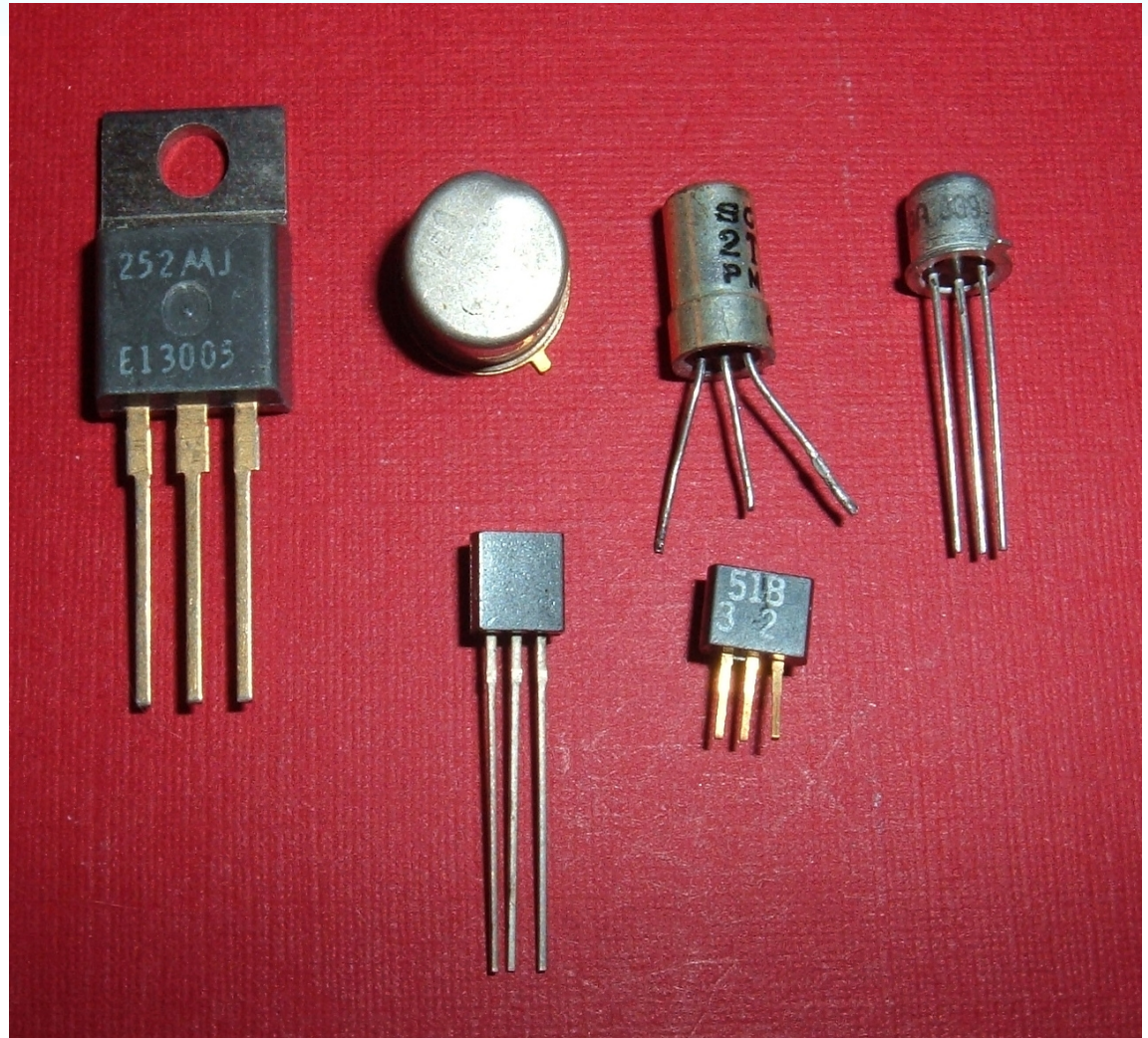


**Figure 4.7** Various representations of a three-input AND gate

# Constructing Gates

- **Transistor** A device that acts, depending on the **voltage level** of an input signal, either as a wire that **conducts** electricity or as a resistor that **blocks** the flow of electricity
  - A transistor has **no moving parts**, yet **acts like a switch**
  - It is made of a **semiconductor** material, which is neither a particularly good conductor of electricity, such as copper, nor a particularly good insulator, such as rubber

# Tube & Transistors

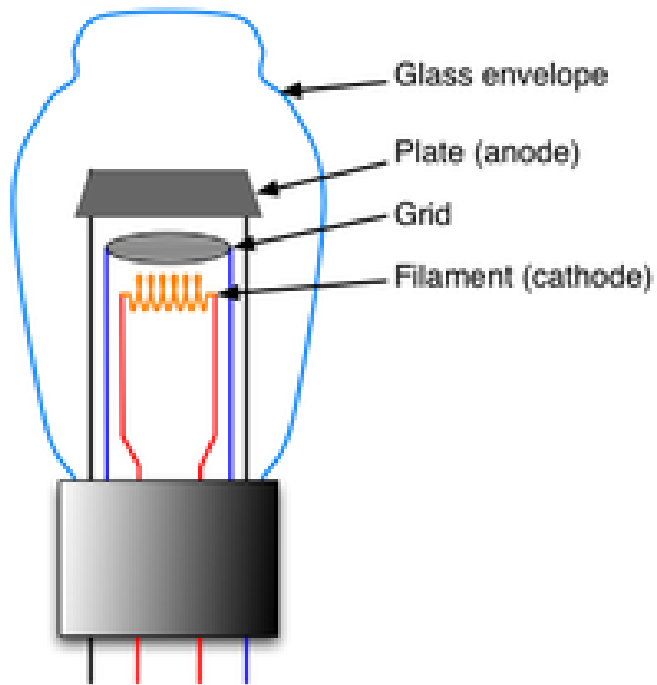

# Constructing Gates

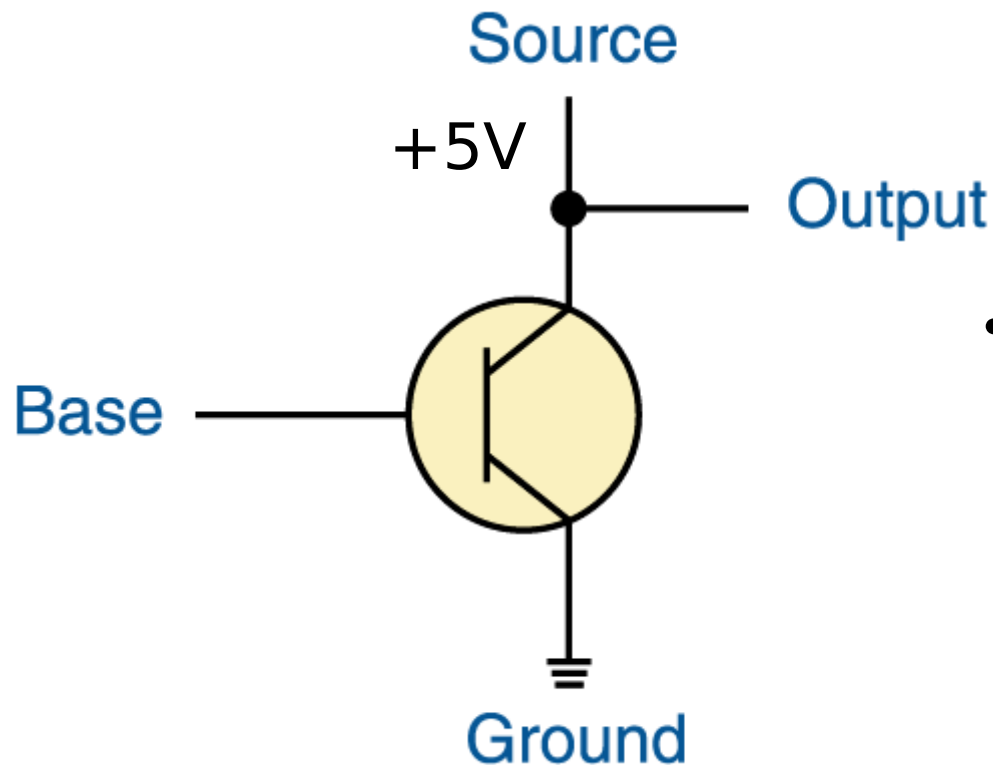


Figure 4.8 The connections of a transistor

- A transistor has **three terminals**
  - A **source**
  - A **base**
  - An **emitter**, typically connected to a ground wire
- If the electrical signal is grounded (**base is high**), it is allowed to flow through an alternative route to the ground (literally) where it can do no harm (**source is low**), **otherwise source is high (+5V)**

# Constructing Gates

- It turns out that, because the way a transistor works, the easiest gates to create are the **NOT**, **NAND**, and **NOR** gates


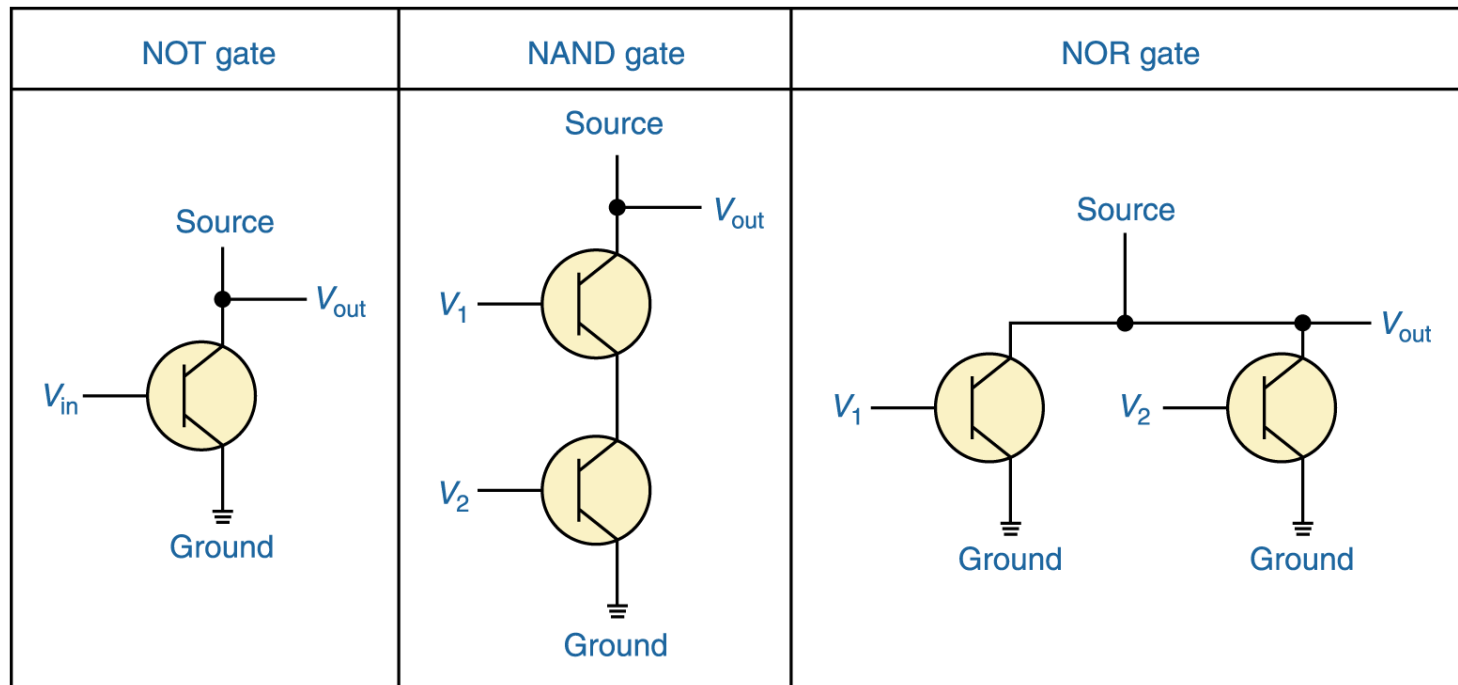



Figure 4.9 Constructing gates using transistors

# Getting Personal

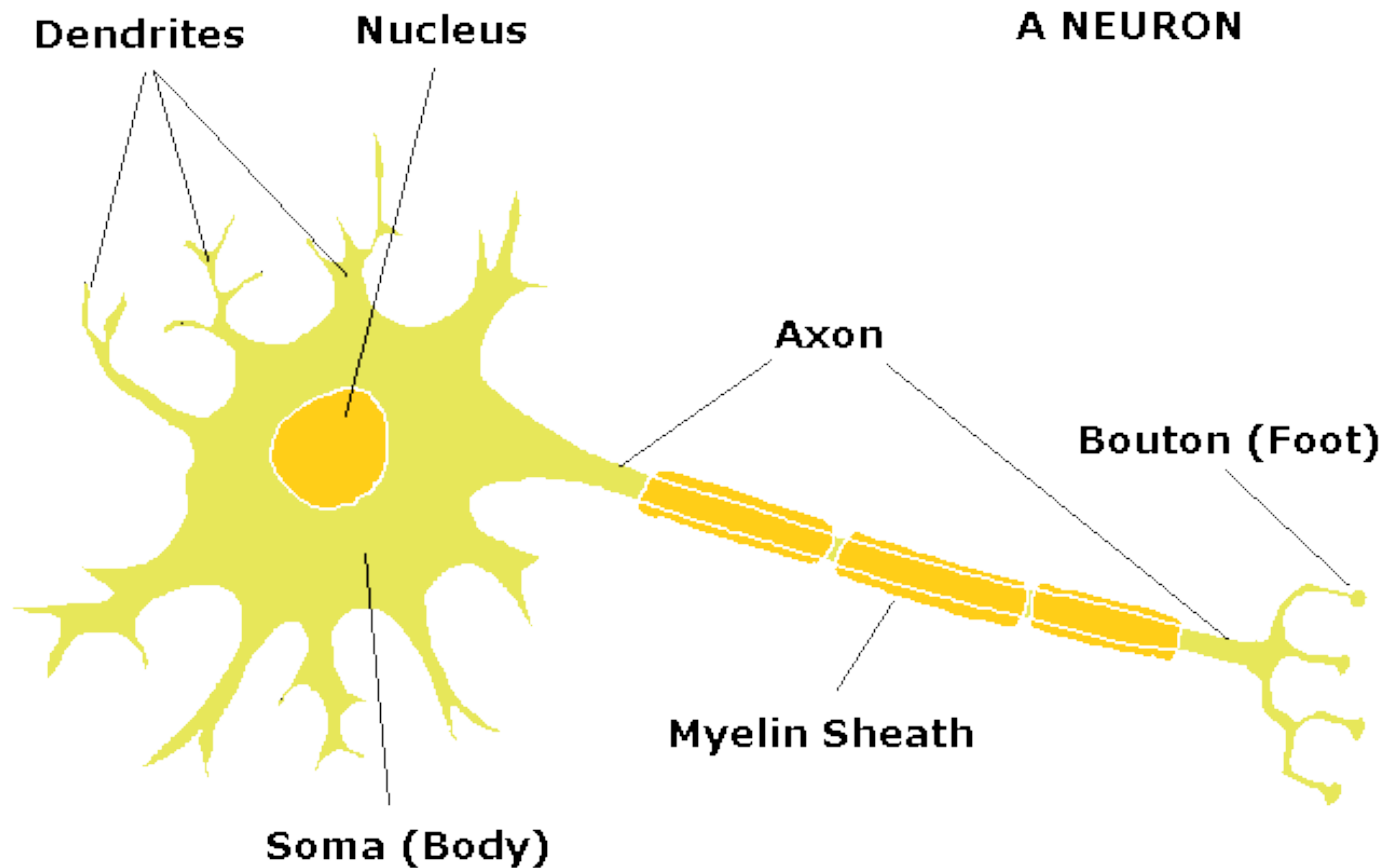

- McCulloch & Pitts – 1943, Artificial Neurons

# Perceptron

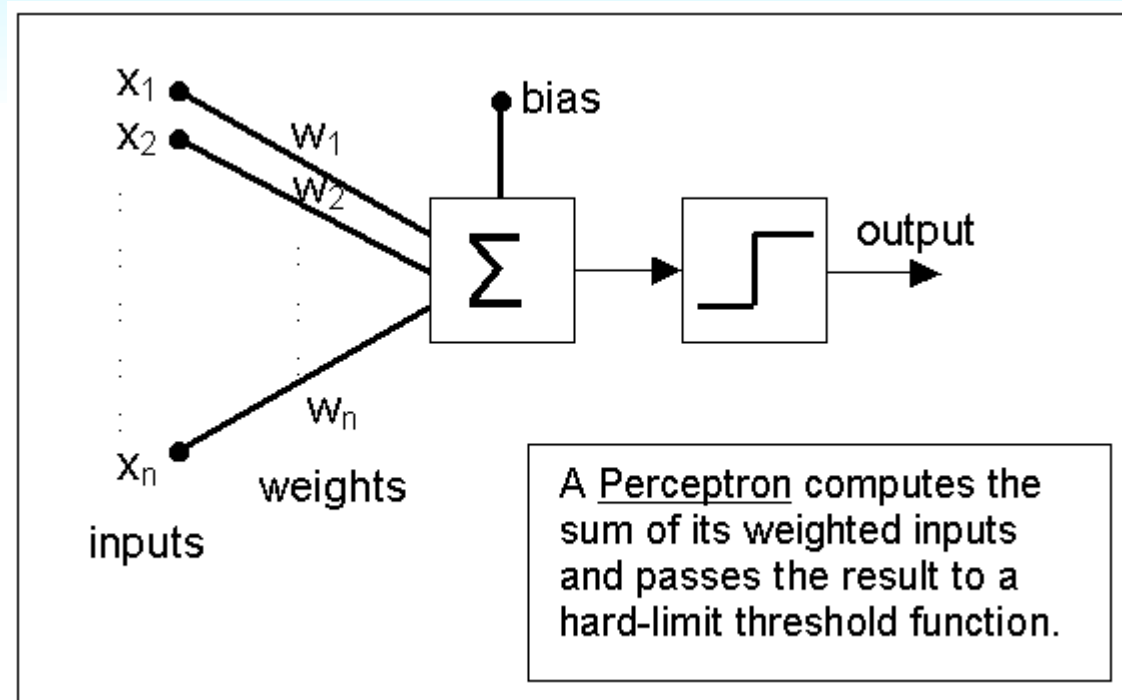

- [Rosenblatt, 1962](#) – Perceptron Learning paper generates great interest
- [Minsky and Papert, 1969](#) – Computational Geometry proof starts a 20 year hiatus in Artificial Intelligence



**“my brain hurts!”**



# Homework

- **Read Chapter Four, Sections 4.1 - 4.3**
- **Exercise: P117, 18-29**

# Assignment One

- **Due Today, Wednesday**
  - No lateness

# Next Class

- **No** Class Monday
- Next Class is Wednesday, 10/4
- Have a Nice Weekend...

